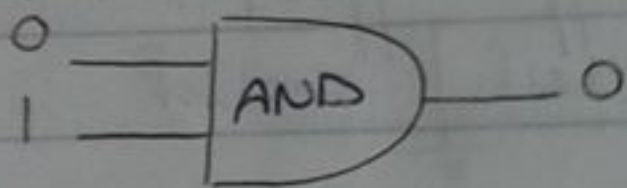


- There are two types of Logic circuits: Combinational Logic circuits and Sequential Logic circuits.

Combinational Logic Circuits

- The output depends only on the current inputs.



Sequential Logic circuits

- The output depends on the current inputs and also on the past sequence of inputs.

- Sequential Logic is Combinational Logic with memory.

- It is divided into Synchronous and asynchronous types.

Asynchronous Seq. Logic


- The state of the device can change at any time in response to changing inputs.

- For example, Latches

* S-R Latch

* D-Latch

- S-R Latch

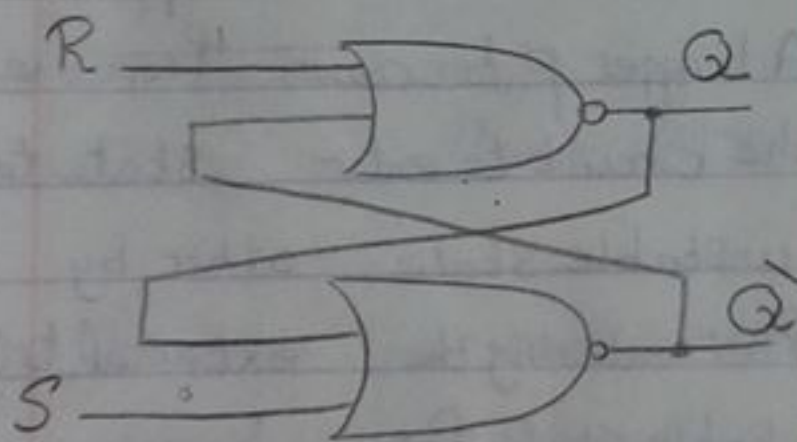

بفرض حالتی
Seq. 11 ↑

	S	R	Q	Q'
	0	0	last Q	last Q'

Reset ← 0 1 0 1

Set ← 1 0 1 0

1 1 0 0

Synchronous Seq. Logic


- The state of the device changes only at discrete times in response to a clock signal.

- Flip-Flops

* S-R Flip-Flop

* D Flip-Flop

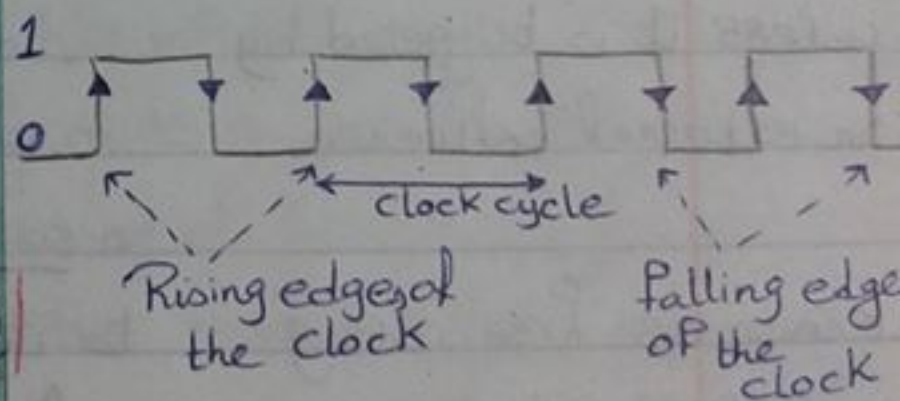- A clock signal is periodic square wave that indefinitely switches values from 0 to 1 and from 1 to 0 at fixed intervals



- The state transition in such circuits occur when only the clock value is 0 or 1 or at the rising or falling edges depending on the type of memory.

- Clock Signals are produced by a single Pulse generator circuit such as a **Multivibrator**.

- Multivibrator is characterized by two amplifying devices (transistors for example) cross-coupled by resistors or capacitors. $\square \square \square \square^H \square \square \square \square$, has two states "High" and "Low"

Multivibrator

Astable

- the circuit is not stable in either states. Continually switches from one state to another
- Stable circuit means it maintains its state unless it is triggered by an external influence
- Known as "Free-running" multivibrator because it alternates between two different output voltage levels during the time it is on.

Monostable


- One of the states is stable but other is unstable
- A trigger pulse causes the circuit to enter the unstable state
- after entering the unstable state for a set time it will return to its stable state.
- useful in creating a timing period of fixed duration in response to some external event.
- Known as "One Shot"

Bistable

- Stable in either state
- Flipped from one state to other by external trigger
- Known as "Flip-flop"
- used to store one bit of info

- Multivibrator is "an electronic circuit used to implement two-state systems such as oscillators, timers & F/Fs".

1] Astable Multivibrator

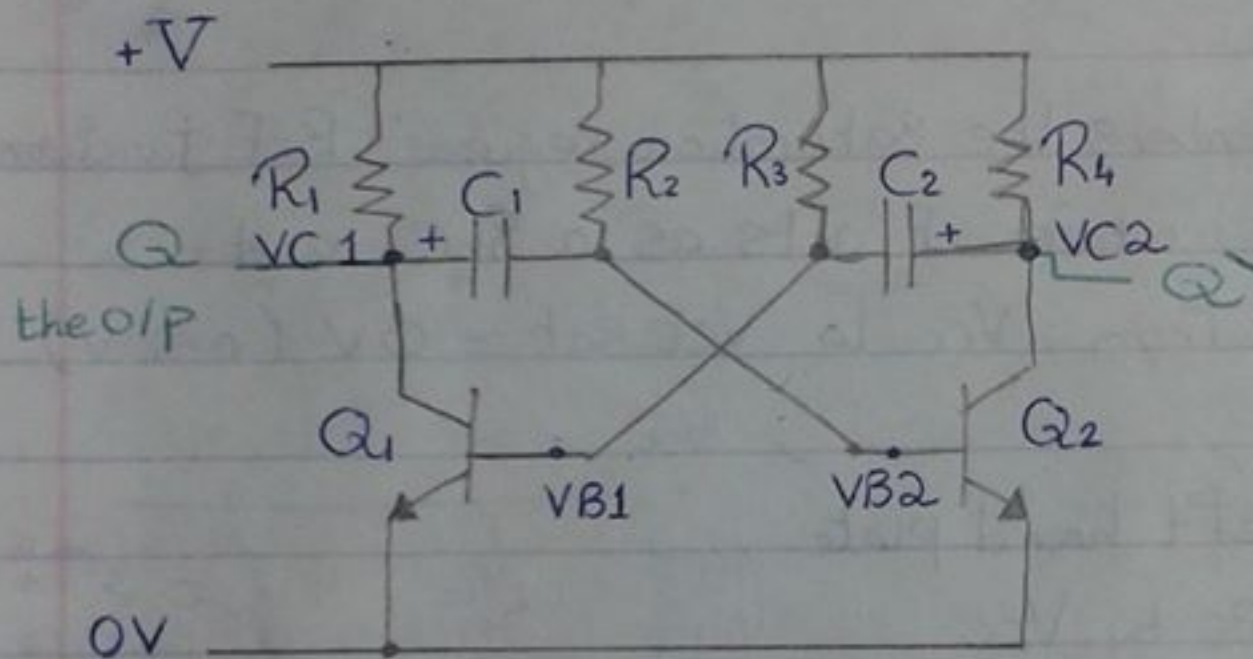

Basic BJT astable multivibrator


- It has two outputs but No inputs.
- drawn in a symmetric form as a cross-coupled pair.
- It is a regenerative ^{circuit} consisting of two amplifying stages connected in a positive feedback loop by two capacitive-resistive coupling networks.
- The amplifying elements may be BJT, FET, vacuum tubes or op-amp.

واضح من المخرج أن الترانزستور يتغير من 1 إلى 2 والعكس
ولا تثبت على State

Operation:


State 1 (Q_1 on, Q_2 off)

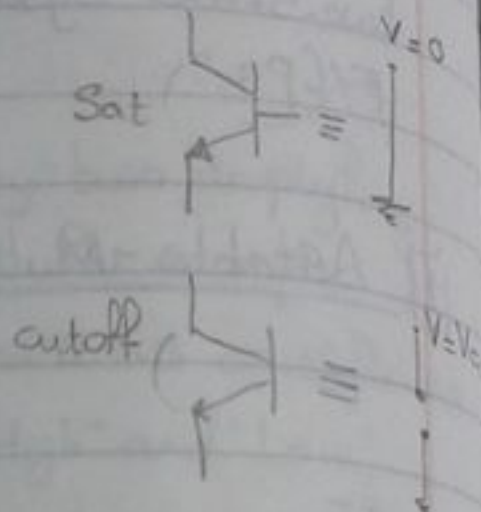- The circuit enters this state when C_2 charges to the point where V_{B1} reaches V_{on} .



- Then Q_1 enters the saturation region (B-E junction is forward) where it acts as a S.C. and pulls V_{C1} from V_{cc} to $V_{CE sat} \approx 0V$ (0.2V).

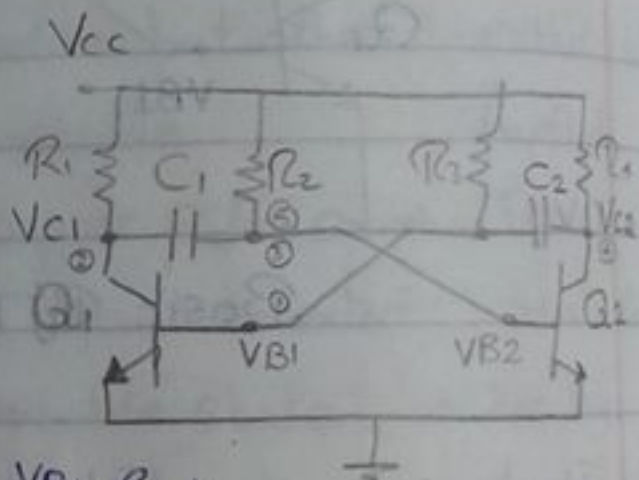- When the left-hand plate of C_1 drops by V_{cc} this will cause an equal and instantaneous drop on the right-hand plate



which will be $V_{cc} - V_{cc}$

was V_{B2} when it was on at State 2.

- Q_2 turns off due to the negative voltage on



its bas

V_{c2} ch
to V_{cc}

depend
 $R_4 C_2$

V_{B2} ch
 R_2 to

(chang
depend

* $R_2 C_1$
the tim
the co
State
because


$V_{B2} =$
State

When
Pulle


the ri
by V

its base.

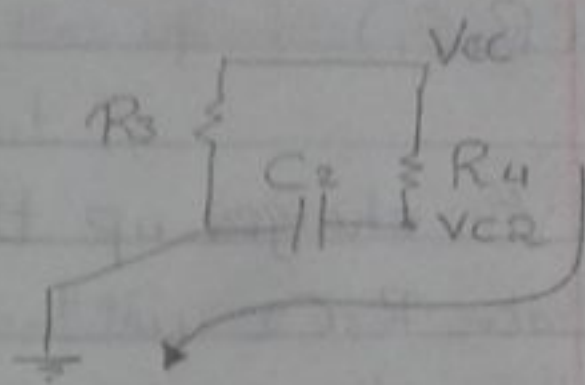
- V_{C2} charges up through R_4 to V_{CC} (charging time depend on the time constant $R_4 C_2$).



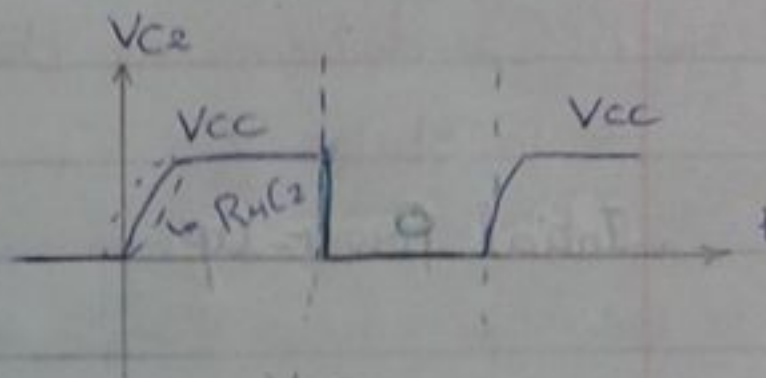- V_{B2} charges up through R_2 towards V_{CC} (charging time depend on $R_2 C_1$).



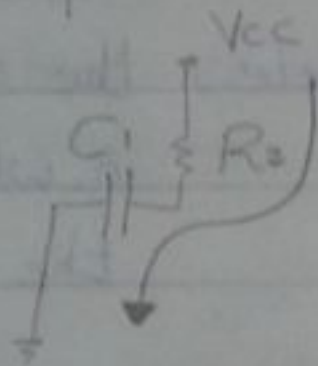- * $R_2 C_1$ determines the time in which the circuit stays in State 1




because the circuit will be in State 2 when $V_{B2} = V_{ON}$.

State 2 (Q_1 off, Q_2 on)


- When V_{B2} reaches V_{ON} , Q_2 turns on and V_{C2} is pulled to 0V.
- the right hand plate of C_2 which is V_{B1} will drop by V_{CC} and it will be $V_{ON} - V_{CC}$.

as Q_1 was on at State 1

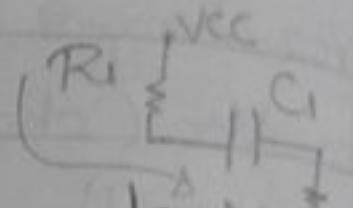• Q_1 turns off due to the negative voltage on its base and V_{C1} charges up to V_{CC} by rate $(R_1 C_1)$.



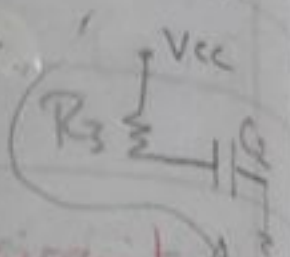• V_{B1} charges up through R_3 towards V_{CC} at rate $R_3 C_2$ until V_{B1} reaches V_{ON} then the circuit enters State 1 again.




• $R_3 C_2$ determines the timeⁱⁿ which the circuit is in State 2.



• Duty Cycle: the ratio between the time duration in which the signal is high to the total period of the signal.

$$D = \frac{t_{on}}{T} \times 100\%$$


$T \rightarrow$ Periodic time

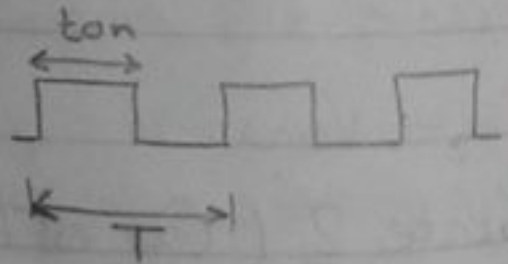

$$D = 50\%$$

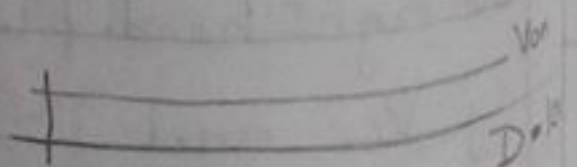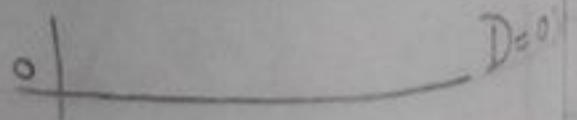

Initial Power-up:

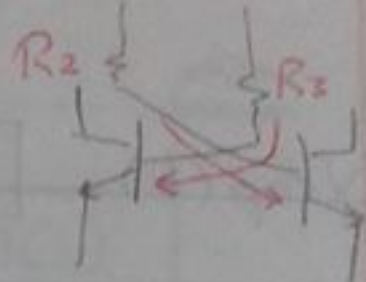


you may ask yourself how will the operation start initially when there is no input?!




- Parasitic capacitors between B and E of Q_1 and Q_2 are charged up towards V_{cc} through R_2 and R_3 . Boths V_{B1} and V_{B2} rise.
- Due to fabrication asymmetries between the two transistors one of them will switch on first and the circuit will be put into one of the above states.

Frequency of Oscillation:

at State ① before Q_2 turns on

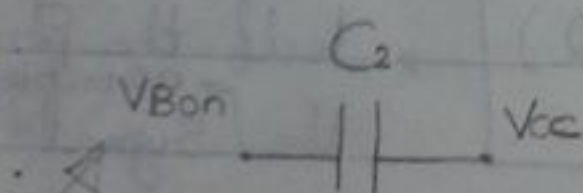

at State ② when Q_2 turns on

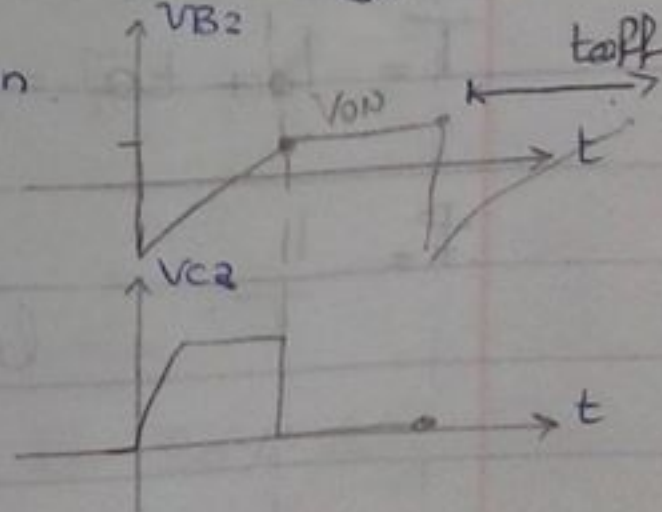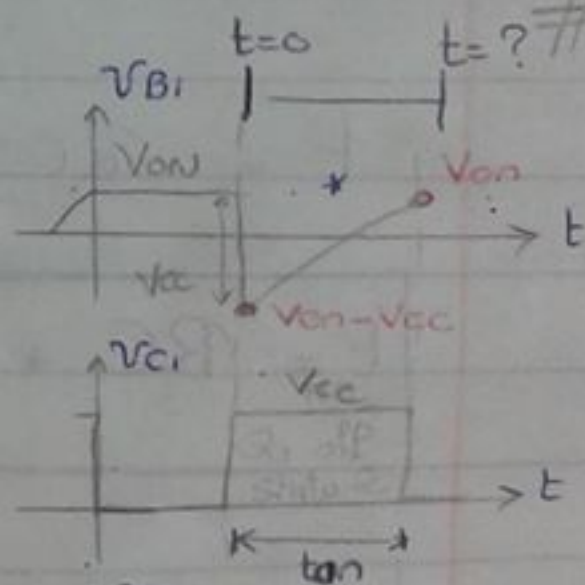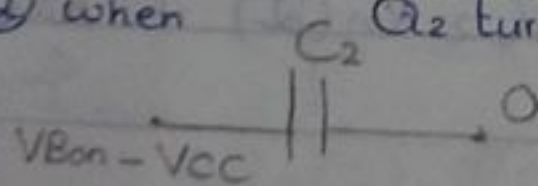

* the capacitor should charge back to V_{ON} .

$$V_{cap}(t) = [(V_{cap\ initial} - V_{charging}) \times e^{-t/RC}] + V_{charging}$$

$$V_{on} = [(V_{on} - V_{cc}) - V_{cc}] e^{-t/RC} + V_{cc}$$

عند $t=0$ يكون $V_{B1} = V_{on}$ يفرض بدأنا t تساوي V_{on} عند $t=0$ عند $V_{on} - V_{cc}$

$$\ln\left(\frac{V_{on} - V_{cc}}{V_{on} - 2V_{cc}}\right) = -\frac{t}{RC}$$

$$t = -RC \cdot \ln\left(\frac{V_{on} - V_{cc}}{V_{on} - 2V_{cc}}\right)$$

$$\therefore V_{on} \ll V_{cc}$$

$$t = -RC \cdot \ln\left(\frac{1}{2}\right)$$

$$t_{on} = RC \cdot \ln(2) \rightarrow \text{half the period of the signal}$$

$$T = t_{on} + t_{off} = R_3 C_2 \ln(2) + R_2 C_1 \ln(2)$$


$$f = \frac{1}{T} = \frac{1}{\ln(2) [R_3 C_2 + R_2 C_1]}$$

$$f \approx \frac{1}{0.693 \cdot (R_2 C_1 + R_3 C_2)}$$

Freq. of oscillation of astable multivibrator

Duty cycle: the ratio between the time duration in which the o/p is high to the total Period of signal.

$$D = \frac{t_{on}}{T} \times 100\%$$

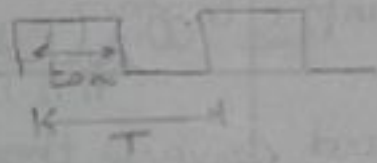

$$\text{if } t_{on} = \frac{1}{2} T$$

$$D = \frac{1}{2} = 50\%$$

For the o/p signal to have a duty cycle of 50% the charging time of C_1 must equal charging time of C_2 .

$$(i.e. R_2 C_1 = R_3 C_2)$$

So practically, $R_2 = R_3$, $R_1 = R_4$, $C_1 = C_2$

$$\text{Hence, } f = \frac{1}{2 \ln(2) \cdot R_3 C_2}$$

$$f = \frac{0.72}{RC}$$



for 50% duty cycle


2 Monostable Multivibrator

• Is a square - or rectangular wave generator with ^{just} one stable condition.



• Sometimes called a One-Shot Multivibrator.

• Basically used for pulse stretching.

• it takes this series of input triggers

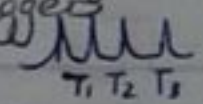

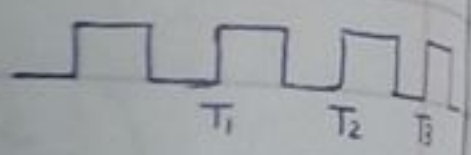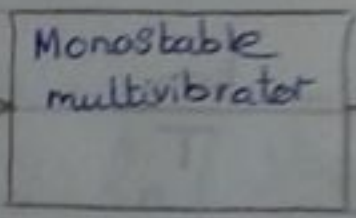
and converts them to uniform square pulses




• used in Computer logic systems and communication navigation equipment.

• The o/p is on Q₂ in contrast to the astable circuit, it has a perfect square waveform. Since the output is not loaded by a capacitor.


• One o/p

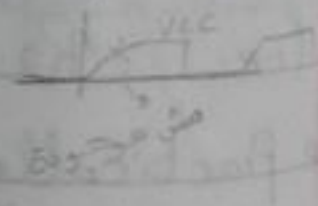

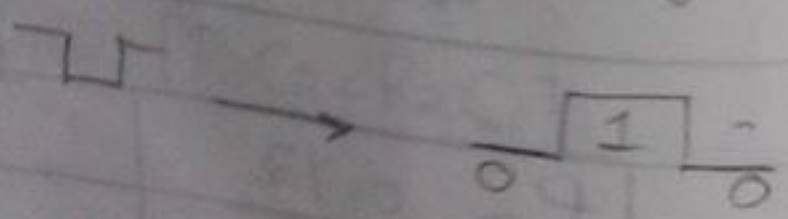one shot because one trigger gate generates one




Operation

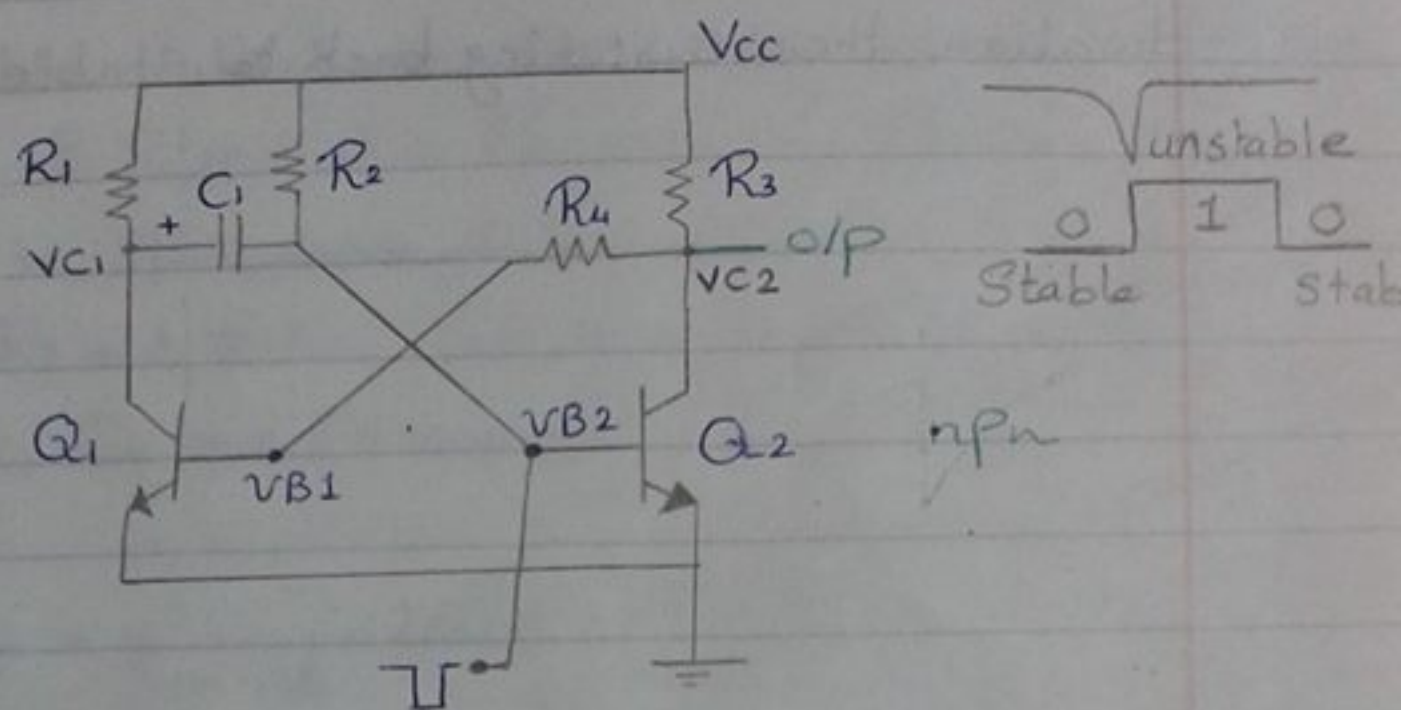

Basic BJT Monostable Multivibrator

- The circuit is Stable at State 2 (Q_1 off, Q_2 on).
- When V_{B2} is triggered by Zero or negative signal, Q_2 becomes off.
- V_{C2} rises to V_{cc} , V_{B1} increases and Q_1 becomes On. \rightarrow thus the circuit is now in State 1.
- V_{C1} Pulled down to 0V.
- When the external signal goes high
- V_{B2} will charge to V_{cc} and it will reach to V_{on} hence, entering State 2 after a time duration $t = \ln(2) R_2 C_1$.
- The circuit remains at State(2) "the Stable State"

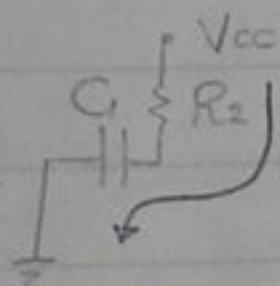

until a trigger event changes that, the circuit then enters the unstable state for a certain duration then switching back to stable state.

Example (1)


t_{on}

t_{off}

(2) next

An astable multivibrator circuit is required to produce a series of pulses at a frequency of 500 Hz with a mark-to-space ratio 1:5.

If $R_3 = R_2 = 100 \text{ k}\Omega$. Calculate the values of the capacitors, C_1 and C_2 required.
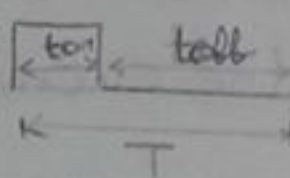
$$T = \frac{1}{f} = \frac{1}{500 \text{ Hz}} = 2 \times 10^{-3} \text{ s.}$$


$$T = t_{on} + t_{off}$$

$$t_{on} = \frac{1}{6} T = 3.33 \times 10^{-4} \text{ sec.}$$

$$t_{off} = \frac{5}{6} T = 1.66 \times 10^{-3} \text{ sec.}$$

$$t_{on} = \ln(2) \cdot R_3 C_2$$

$$C_2 = \frac{1.66 \times 10^{-3}}{0.69 \times 100 \text{ k}\Omega} = 4.83 \times 10^{-9} \text{ F} = 4.83 \text{ nF.}$$

$$C_1 = \frac{3.33 \times 10^{-4}}{0.69 \times 100 \text{ k}\Omega} = 2.41 \times 10^{-8} \text{ F} = 24.1 \text{ nF.}$$

3 Bistable Multivibrator


- have two Stable States!

- Trigger is needed to change the state to the other state and then another trigger is needed to return the circuit to the first state.

- The trigger doesn't have to be of fixed frequency.

- Both Capacitive-resistive networks are replaced by resistive networks.


- Note

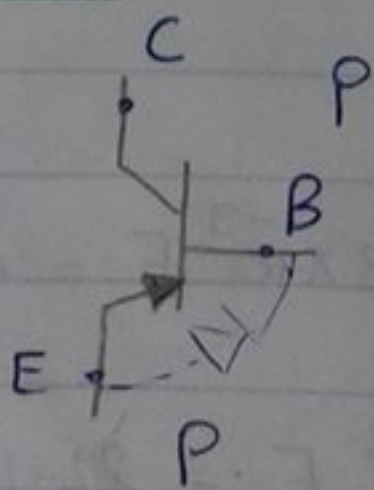

$n \rightarrow$ to be on

$$V_E \geq V_B + V_{on}$$
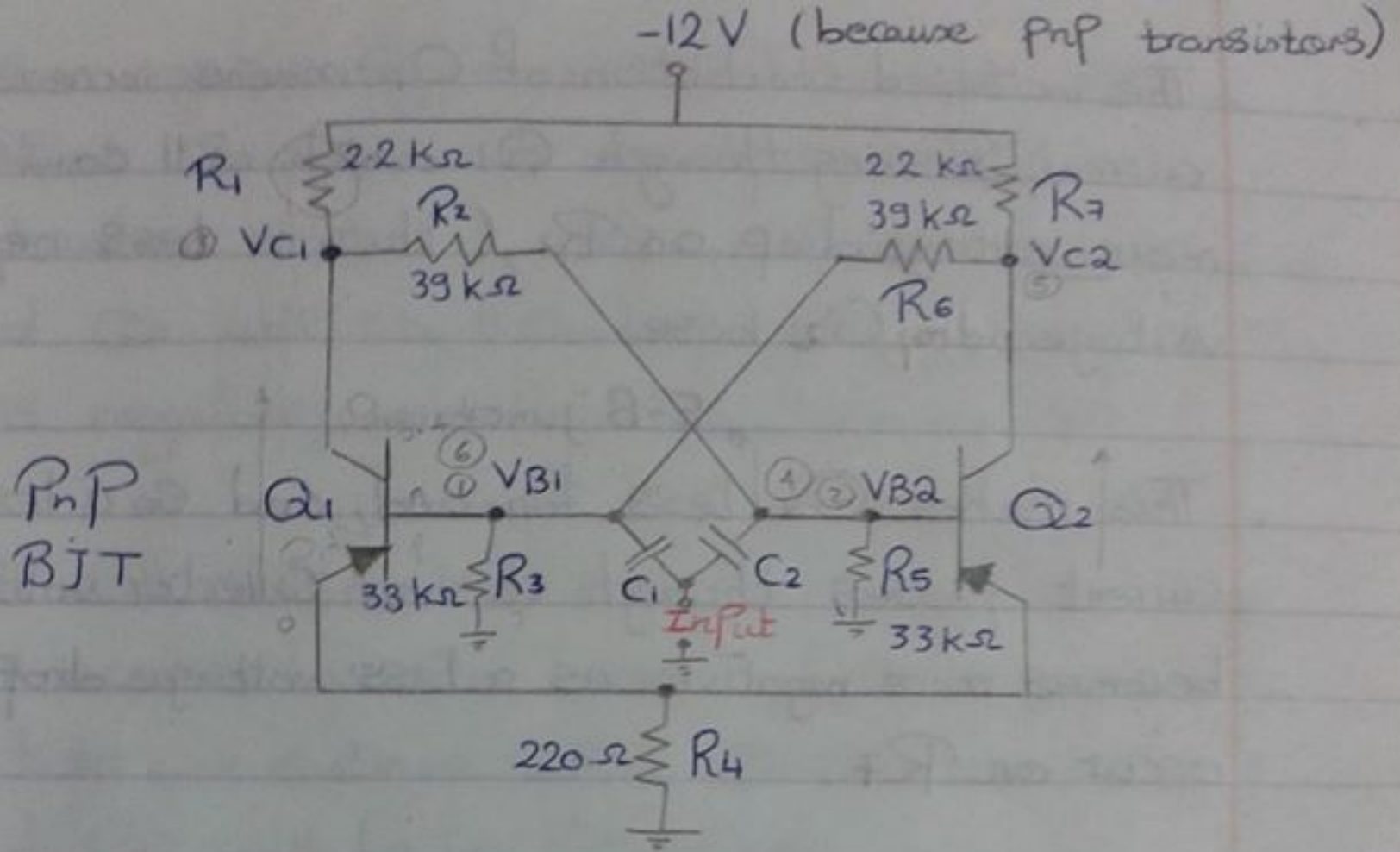
$$\text{if } V_E = 0 \rightarrow V_B \leq -V_{on}$$
$$V_B \leq -0.7$$




Operation

- When Power is first applied, the voltage divider networks (R_1, R_2, R_5 for Q_2 and R_7, R_6, R_3 for Q_1) places negative voltage on the bases of Q_1 & Q_2 .

- Both transistors start to conduct.

- Due to Slight difference between the two circuits (tolerance), one transistor will conduct more than the other.

- Assume Q_1 conducts more than Q_2

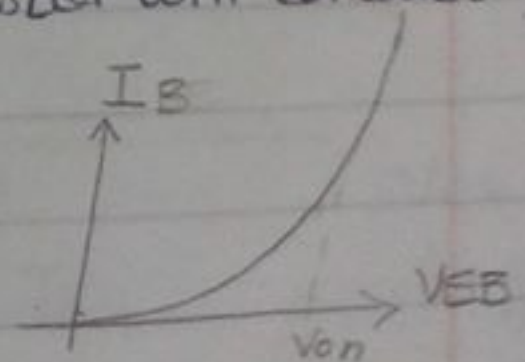

- The increased conduction of Q_1 means increased current passing through Q_1 which will cause more voltage drop on R_1 , thus a less negative voltage on Q_2 base.

E-B junction


- This makes Q_2 less forward and so a less current passes through it and collector voltage becomes more negative as a less voltage drop will occur on R_2 .

- The more negative voltage of V_{C2} is coupled to V_{B1} through the voltage divider network. So, Q_1 will conduct even more heavily.

- This is called regenerative action that will continue until Q_2 is cutoff and Q_1 is saturated.


- The circuit is in a stable state and remains there until trigger is applied to switch the state.

- When negative trigger is applied now, it will not affect Q_1 as it is already conducting and in Saturation but V_{B2} will be more negative and Q_2 will start conducting and V_{C2} will be less negative which is the same as V_{B1} .
- Q_1 will conduct less current, negative voltage will increase on Q_2 base and the regenerative action will continue until Q_1 will be in cutoff and Q_2 will be in Saturation.
- Another negative trigger will cause the circuit to switch to the other state.

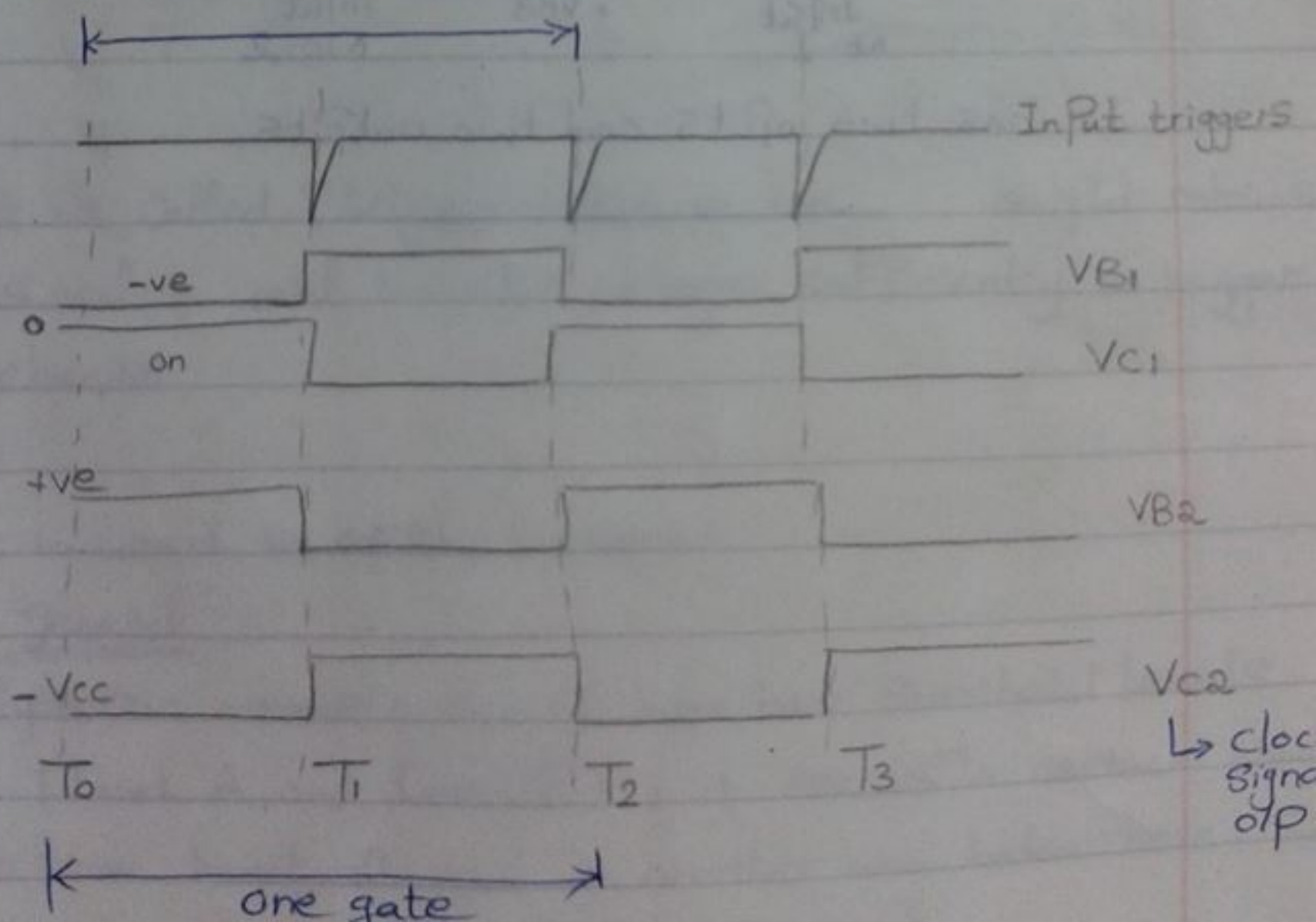

- F/Fs used as Counters, Shift-Registers, clock Pulse generators and in memory circuits


• Another Circuit:

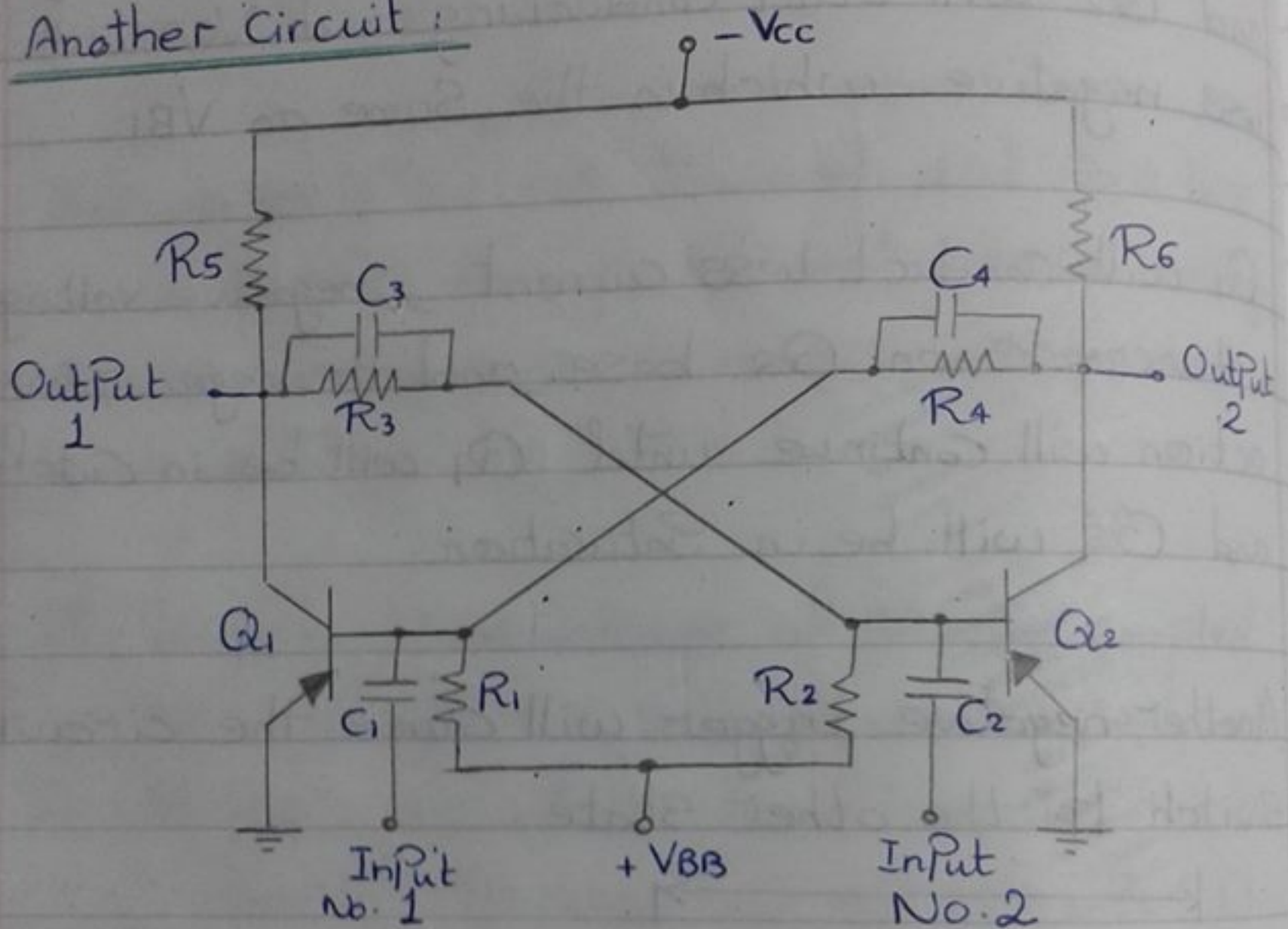

- It has two inputs and two outputs.

Schmitt Trigger

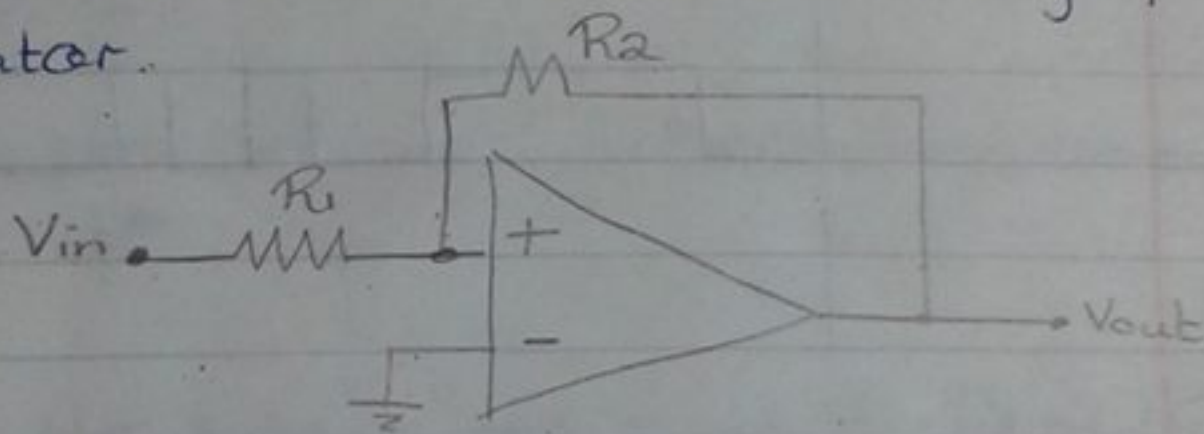- A decision-making circuit used to convert a slowly varying analogue signal into one of two possible binary states depending on whether the analogue voltage is above or below threshold values.
- It is a Comparator circuit with hysteresis implemented by applying positive feedback to the non-inverting i/p of a Comparator.




- It is called "trigger" because the output retains its value until the input changes sufficiently to trigger a change.
- It is used to apply hysteresis.


In general

- Hysteresis means (a circuit have two threshold levels (Level A and Level B), it reactsⁱⁿ a certain way above Level A and in another way below Level B but in between it doesn't react).

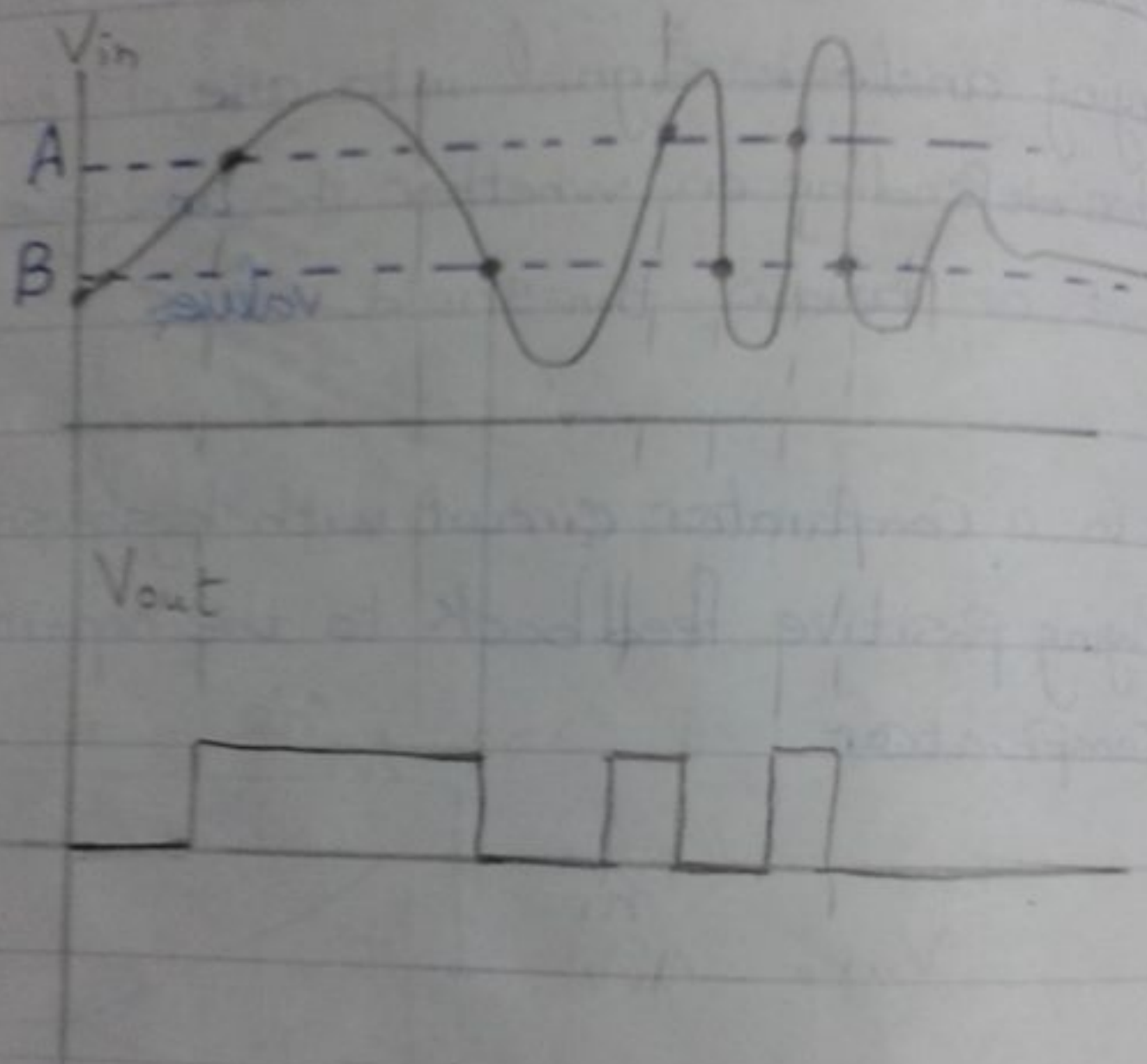
Here, if $V_{in} > \text{Level A} \rightarrow \text{o/p is H}$
 $V_{in} < \text{Level B} \rightarrow \text{o/p is L}$



Schmitt trigger Symbol

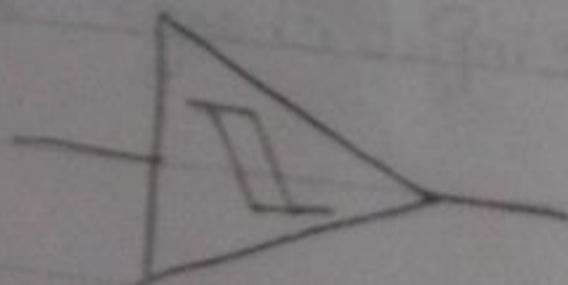

• Two-transistor Schmitt trigger:

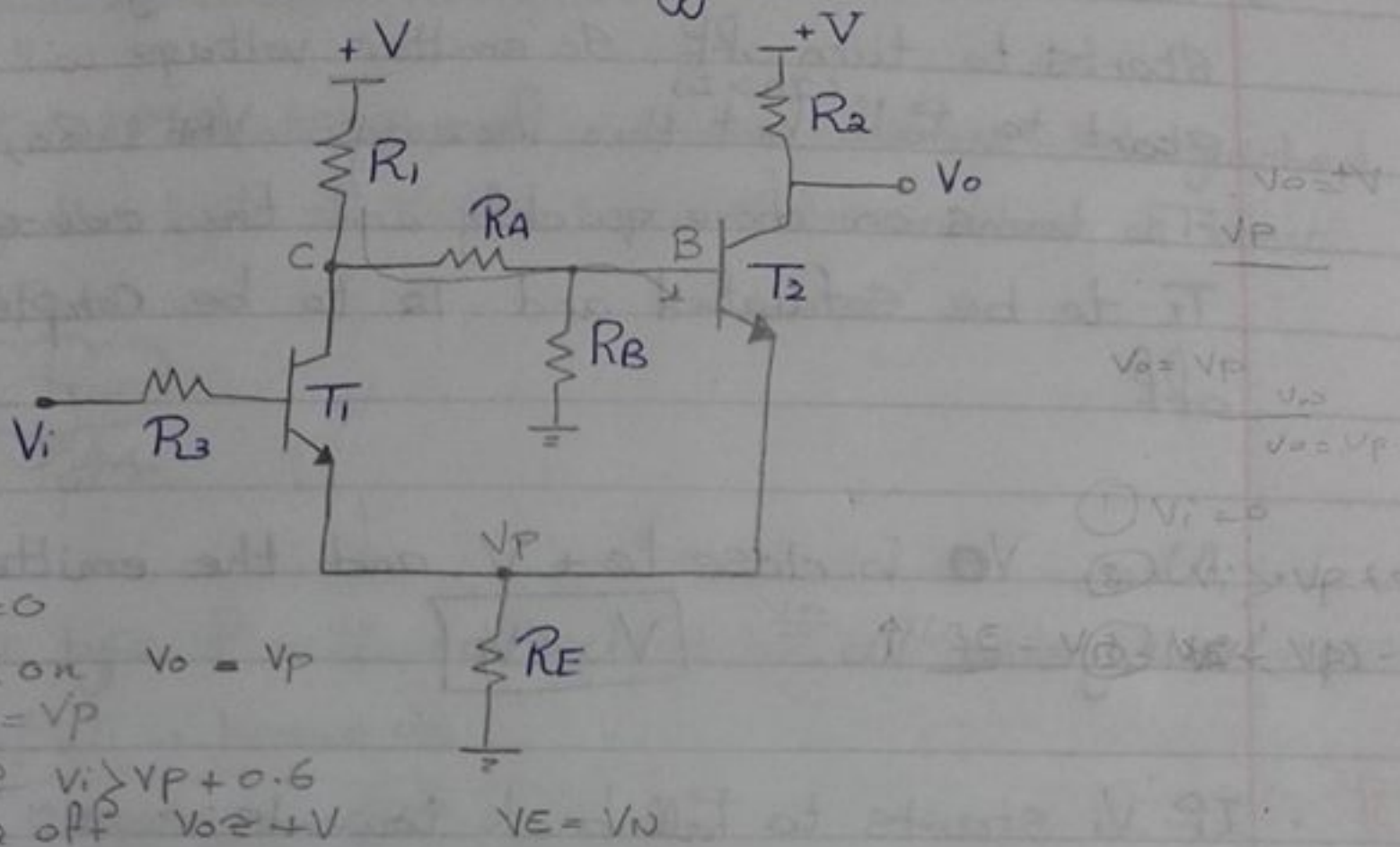

- ① $V_i = 0$
- ② T_2 on $V_o = V_p$
- ③ $V_E = V_p$
- ④ If $V_i > V_p + 0.6$
- ⑤ T_2 off $V_o \approx +V$ $V_E = V_N$

1. If V_i is close to Zero, T_1 has no base current so it is off.

• T_2 draws the base current through R_1 , R_A and R_B so it is On. (Saturated) and acts as a S.C.

• V_o sits at the mid-point of R_2 , R_E potential divider somewhere between $+V$ and $\frac{1}{2} \cdot (V_p)$.

2. If V_i starts to increase and emitter voltage is held at a fixed value by current through T_2 . When V_i increases about 0.6 above this value (V_p)

(not S.C.)
• T_1 starts to conduct as it does, ~~the~~ T_2

• The base current of T_2 starts decreasing and T_2 starts to turn off. So emitter voltage will start to fall ^($I_A > I_1$) but this increases V_{BE1} so, T_1 turns on more quickly and this causes T_1 to be saturated and T_2 to be completely off.

• Now, V_o is close to $+V$ and the emitter voltage is V_N . $V_N < V_P$

[3] • If V_i starts to fall back towards zero. V_i has fallen to about 0.6 V above this value (call it V_N).

• T_1 will start to turn off so T_2 will begin to turn on so V_E will increase and this will let T_1 turn off more quickly returning V_o to V_P .

• The difference between the two thresholds is called hysteresis.

7- What is the type of the multivibrator shown in the previous figure and what is the idea of its operation?

